


PAPER – II
ELECTRONICS

Note : Attempt all the questions. Each question carries *two* (2) marks.

1. A MOS capacitor made using *p* type substrate is in the accumulation mode. The dominant charge in the channel is due to the presence of
 - 1) holes
 - 2) electrons
 - 3) positively charged ions
 - 4) negatively charged ions


2. Norton's theorem states that a complex network connected to a load can be replaced with an equivalent impedance
 - 1) in series with a current source
 - 2) in parallel with a voltage source
 - 3) in series with a voltage source
 - 4) in parallel with a current source

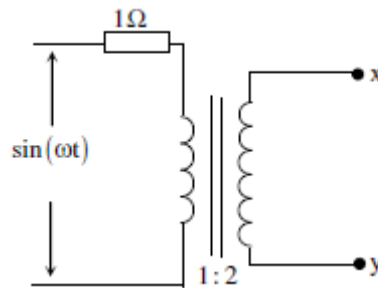3. Assuming an ideal transformer. The Thevenin's equivalent voltage and impedance as seen from the terminals *x* and *y* for the circuit in figure are




- 1) $2 \sin(\omega t)$, 4Ω
 - 2) $1 \sin(\omega t)$, 1Ω
 - 3) $1 \sin(\omega t)$, 2Ω
 - 4) $2 \sin(\omega t)$, 0.5Ω
-
4. If $X(s)$, the Laplace transform of signal $x(t)$ is given by $X(s) = \frac{(s + 2)}{(s + 1)(s + 3)^2}$, then the value of $x(t)$ as $t \rightarrow \infty$ is
 - 1) 0
 - 2) ∞
 - 3) 100
 - 4) can't be determined

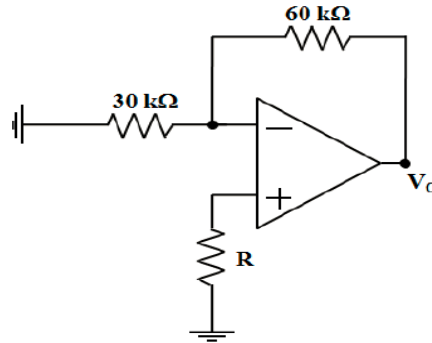5. In the circuit given below, each input terminal of the opamp draws a bias current of 10 nA. The effect due to these input bias currents on the output voltage V_o will be zero, if the value of R chosen in kilo-ohm is



- 1) 20
- 2) 30
- 3) 60
- 4) 90

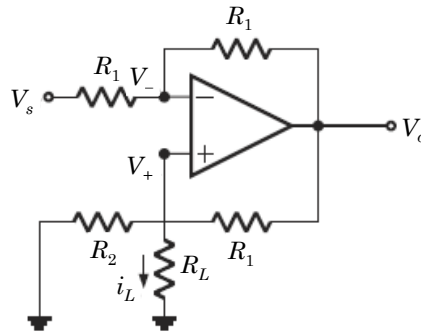6. In the op amp circuit given below, the load current i_L is




- 1) $-\frac{V_s}{R_2}$
 - 2) $\frac{V_s}{R_2}$
 - 3) $-\frac{V_s}{R_L}$
 - 4) $\frac{V_s}{R_1}$
7. A low – pass filter with a cut-off frequency of 30 Hz is cascaded with a high-pass filter with a cut-off frequency of 20 Hz. The resultant system of filters will function as
- 1) an all-pass filter
 - 2) an all-stop filter
 - 3) an band stop (band-reject) filter
 - 4) a band-pass filter

8. In which 'T' state, the 8085 microprocessor sends address to memory or I/O and activate 'ALE' signal?
- 1) T1
 - 2) T2
 - 3) T3
 - 4) T4
9. How many bytes of bit addressable memory are present in 8051 based microcontrollers?
- 1) 8 bytes
 - 2) 16 bytes
 - 3) 32 bytes
 - 4) 64 bytes
10. In which of the following priority interrupt controller 8259A, the interrupt requests are registered?
- 1) ISR
 - 2) IRR
 - 3) IMR
 - 4) Priority resolver
11. How many I/O spaces on the I/O map are required for interfacing a DMA controller in an 8085 system?
- 1) 4
 - 2) 8
 - 3) 16
 - 4) 64
12. _____ is the process of using the same name for two or more functions.
- 1) Function Overloading
 - 2) Operator Overloading
 - 3) Default Function
 - 4) Constructors

13. A magnetron is operated at a duty cycle of 0.001. It has a peak power output of 100 kilowatts. Its average power is
- 1) 10,000 watts
 - 2) 100 watts
 - 3) 1,000 watts
 - 4) 1,000,000 watts
14. What is the carrier frequency in an AM wave when its highest frequency component is 850 Hz and the bandwidth of the signal is 50 Hz?
- 1) 80 Hz
 - 2) 695 Hz
 - 3) 625 Hz
 - 4) 825 Hz
15. In statistical Time-Division Multiplexing (TDM), a block of data is usually many bytes while address is just
- 1) many bytes
 - 2) few bytes
 - 3) zero byte
 - 4) infinity bytes
16. In an FM stereo multiplex transmission, the
- 1) sum signal modulates 19 kHz subcarrier
 - 2) difference signal modulates the 19 kHz subcarrier
 - 3) difference signal modulates the 38 kHz subcarrier
 - 4) difference signal modulates the 67 kHz subcarrier
17. What type of fiber has the highest modal dispersion?
- 1) Step-index multimode
 - 2) Graded index multimode
 - 3) Step-index single mode
 - 4) Graded index mode

18. The typical ratio of latching current to holding current in a 20A thyristor is
- 1) 5.0
 - 2) 2.0
 - 3) 1.0
 - 4) 0.5
19. In a step-down chopper using pulse-width modulation with $T_{ON} = 3 \times 10^{-3}$ s and $T_{OFF} = 3 \times 10^{-3}$ s periods. The chopping frequency in Hz is
- 1) 333.33
 - 2) 250
 - 3) 500
 - 4) 1000
20. Which one of the following instruments is an integrating instrument?
- 1) ammeter
 - 2) voltmeter
 - 3) wattmeter
 - 4) watt-hour meter
21. For signal conditioning of a piezoelectric type transducer we require
- 1) a charge amplifier
 - 2) a differential amplifier
 - 3) an instrumentation amplifier
 - 4) a transconductance amplifier

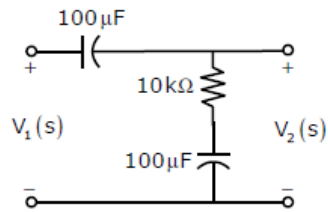22. The transfer function $\frac{V_2(s)}{V_1(s)}$ of the circuit shown below is



- | | |
|--|--|
| <p>1) $\frac{0.5s + 1}{s + 1}$</p> <p>3) $\frac{s + 2}{s + 1}$</p> | <p>2) $\frac{3s + 6}{s + 2}$</p> <p>4) $\frac{s + 1}{s + 2}$</p> |
|--|--|
23. For a stable system
- 1) gain margin must be positive but phase margin can be positive or negative
 - 2) phase margin must be positive but gain margin can be positive or negative
 - 3) both gain margin and phase margin must be positive
 - 4) one of them must be zero

24. In a type-1 second order system, the first undershoot occurs at a time

- 1) $t_p = \frac{\pi}{\omega_d}$
- 2) $t_p = \frac{2\pi}{\omega_d}$
- 3) $t_p = \frac{\pi}{2\omega_d}$
- 4) $t_p = \frac{\omega_d}{2\pi}$

25. Due to an increase in the forward path gain of a control system, the maximum overshoot is

- 1) reduced
- 2) increased
- 3) not affected
- 4) eliminated

26. Current through a PN junction diode in reverse biased condition is due to

- 1) minority carriers
- 2) majority carriers
- 3) both majority and minority carriers
- 4) can't be determined

27. In CMOS technology, shallow P-well or N-well regions can be formed using

- 1) low pressure chemical vapor deposition
- 2) low energy sputtering
- 3) low temperature dry oxidation
- 4) low energy ion-implantation


28. When a JFET is cut-off, the depletion layers are

- 1) far apart
- 2) close together
- 3) touching
- 4) conducting


29. In bipolar transistors, dc current gain is

- 1) $\frac{I_C}{I_E}$
- 2) $\frac{I_C}{I_B}$
- 3) $\frac{I_E}{I_B}$
- 4) $\frac{I_E}{I_C}$

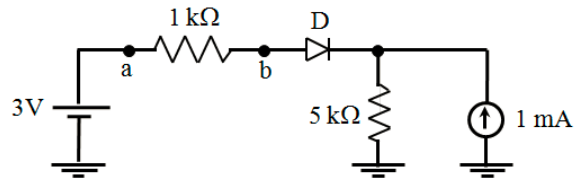30. The diode D used in the circuit below is ideal. The voltage drop V_{ab} across the $1\text{k}\Omega$ resistor in volt is




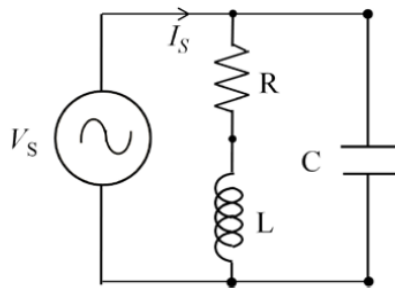- 1) 0
 - 2) 2
 - 3) 3
 - 4) 5
31. In the circuit shown below, $V_s = 101 \angle 0^\circ \text{ V}$, $R = 10\Omega$ and $\omega L = 100\Omega$. The current I_s is in phase with V_s . The magnitude of I_s in milliamperes is



- 1) 1
 - 2) 10
 - 3) 100
 - 4) 1000
32. The parameter that indicates how fast the output of an op amp can vary for the input variations is
- 1) slew rate
 - 2) unity gain bandwidth
 - 3) open loop gain
 - 4) offset voltage

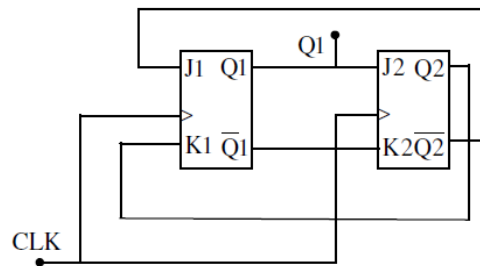33. The outputs of two flip-flops Q1, Q2 in the figure shown are initialized to 0, 0. The sequence generated at Q1 upon application of clock signal is



- 1) 01110.....
 - 2) 01010.....
 - 3) 00110.....
 - 4) 01100.....
34. The SOP (sum of products) form of a Boolean function is $\Sigma(0,1,3,7,11)$, where inputs are A, B, C, D (A is MSB, and D is LSB). The equivalent minimized expression of the function is
- 1) $(\bar{B} + C)(\bar{A} + C)(\bar{A} + \bar{B})(\bar{C} + D)$
 - 2) $(\bar{B} + C)(\bar{A} + C)(\bar{A} + \bar{C})(\bar{C} + D)$
 - 3) $(\bar{B} + C)(\bar{A} + C)(\bar{A} + \bar{C})(\bar{C} + \bar{D})$
 - 4) $(\bar{B} + C)(A + \bar{B})(\bar{A} + \bar{B})(\bar{C} + D)$
35. Which of the following types of ADC requires S/H?
- 1) Successive approximation type
 - 2) Integration type
 - 3) Flash
 - 4) Sigma-Delta
36. The present output Q_n of an edge triggered JK flip-flop is logic 0. If $J = 1$, then Q_{n+1}
- 1) Cannot be determined
 - 2) Will be logic 0
 - 3) Will be logic 1
 - 4) Will rave around

37. What will be the output of the following code segment?

```
main() {  
char s[10];  
strcpy(s, "abc");  
printf("%d %d", strlen(s), sizeof(s));  
}
```

- 1) 3 10
- 2) 3 3
- 3) 10 3
- 4) 10 10

38. Set precision requires the _____ header file.

- 1) stdlib.h
- 2) iomanip.h
- 3) console.h
- 4) conio.h

39. A wave is incident normally on a good conductor. If the frequency of a plane electromagnetic wave increases four times, the skin depth, will


- 1) increase by a factor of 2
- 2) decrease by a factor of 4
- 3) remain the same
- 4) decrease by a factor of 2

40. Poynting vector gives

- 1) direction of polarization
- 2) rate of energy flow
- 3) intensity of electric field
- 4) intensity of magnetic field

41. What is the typical wavelength of light emitted from epitaxially grown LEDs?
- 1) 840 nm
 - 2) 490 nm
 - 3) 480 nm
 - 4) 940 nm
42. Chromatic dispersion can be eliminated by
- 1) using a monochromatic light source
 - 2) using a very small numerical aperture fiber
 - 3) using a graded-index fiber
 - 4) using a very sensitive photo detector
43. In a regulated power supply, two similar 15 V Zeners are connected in series. The input voltage is 45 V DC. If each Zener has a maximum current rating of 300 mA, what should be the value of the series resistance?
- 1) 10 Ω
 - 2) 20 Ω
 - 3) 40 Ω
 - 4) 50 Ω
44. Which one of the following regulators has the highest efficiency?
- 1) Shunt regulator
 - 2) Series regulator
 - 3) Switching regulator
 - 4) DC-DC converter
45. The slip of an induction motor normally does not depend on
- 1) rotor speed
 - 2) synchronous speed
 - 3) shaft torque
 - 4) core-loss component

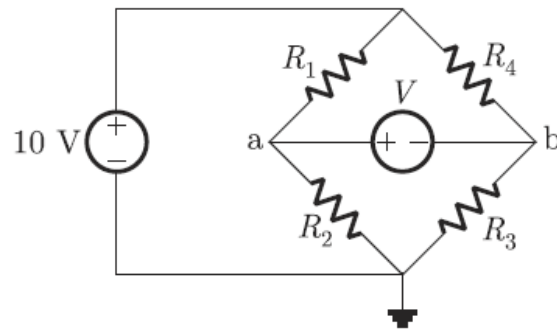46. If $R_1 = R_2 = R_4 = R$ and $R_3 = 1.1R$ in the bridge circuit shown in the figure, then the reading in the ideal voltmeter connected between a and b is,



- | | |
|-------------|------------|
| 1) 0.238 V | 2) 0.138 V |
| 3) -0.238 V | 4) 1 V |
47. Liquid flow rate is measured using
- 1) Pirani gauge
 - 2) Pyrometer
 - 3) Orifice plate
 - 4) Bourdon tube
48. The input impedance of CRO is equivalent to a $1\text{ M}\Omega$ resistance in parallel with a 45 pF capacitance. It is used with a compensated 10-1 attenuation probe. The effective input capacitance at the probe tip is
- 1) 4.5 pF
 - 2) 5 pF
 - 3) 45 pF
 - 4) 450 pF
49. In a block diagram representation of a system, three blocks with gains 5, 8 and 4 are connected in cascade. The total gain of the arrangement is
- | | |
|--------|-------|
| 1) 8 | 2) 17 |
| 3) 160 | 4) 52 |
50. Inverse Laplace transform of $\frac{1}{(s+a)}$ is
- 1) e^{-at}
 - 2) e^{+at}
 - 3) $1 - e^{-at}$
 - 4) $1 + e^{-at}$

ROUGH WORK

ROUGH WORK