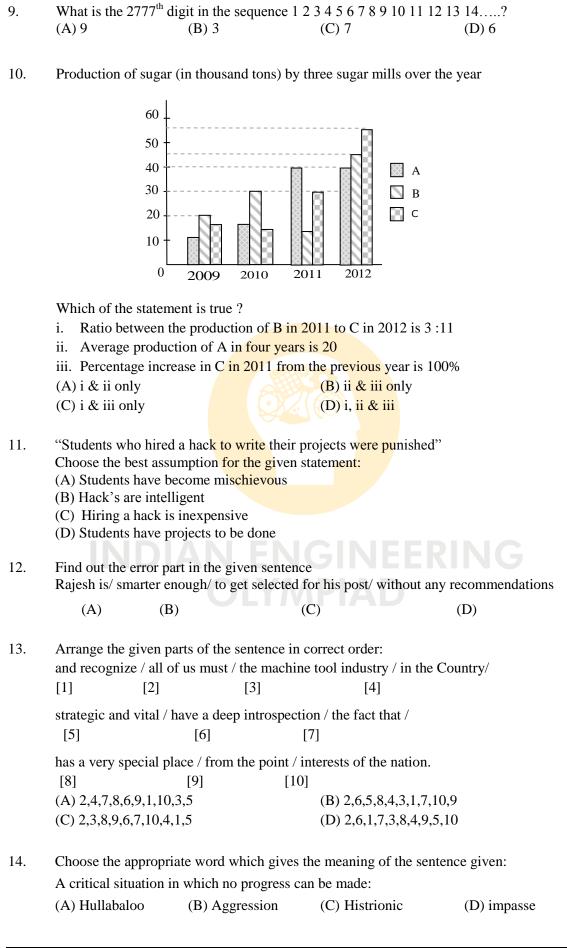


## **Section-I: General Aptitude**

1.	The values of x which satisfy $(x-1)(x)(x+1) \le 0$ is / are						
	i. $x \le 0$ ;	ii. $x \le -1$	iii. $0 \le x \le 1$				
	(A) Only I	(B) Both ii and iii	(C) Both i and ii	(D) Both i and iii			
2.	A company awarded annual bonuses to its employees. Of the employees at the company 70% received bonuses of at least 10,000, 40% received bonuses of at least 50,000, an 20% received bonuses of at least 1,00,000. If 60 employees received bonuses of less tha 10,000, how many employees received bonuses of at lest 50,000 but less than 1,00,000?  (A) 80  (B) 50  (C) 48  (D) 40						
3.	A sum of money compounded annually amounts to thrice itself in 10 years. In how many years, will it become 9 times itself?						
	(A) 6	(B) 8	(C) 10	(D) 12			
4.	Babita was asked to calculate the arithmetic mean of ten positive two digit integers. By mistake, she interchanged the two digits, say t and u, in one of these ten integers. As a result, her answer for the arithmetic mean was 1.8 more than what it should have been. Then u - t equals						
	(A) 1	(B) 2	(C) 3	(D) 4			
5.	Operating togeth How many hours (A) 18	, Tap A takes twice as her at their respective cons would it take the Tap A  (B) 9	stant rates, the taps ca to fill the tank operatin (C) 12	n fill the tank in 6 hours.  ng alone?  (D) 15			
6.	A shopkeeper sells two items at the price of Rs.160. If one of them is sold at 10% profit and another sold at 10% loss, then find the profit/loss?						
	(A) 3.23	(B) 5.75	(C) 2.5	(D) 6.9			
7.	The sum of ages of 5 children born at interval of 3 years each is 50 years. What is the age of youngest child?						
	(A) 10	(B) 2	(C) 7	(D) 4			
8.	The cost of the components x, y, z of a machine worth Rs.45,000 in 1996 is given as a pie chart? In the following year, the cost of the components x, y, z increased by 10%, 30%, and 20% respectively. What is the cost of the machine in 1997?						
	(A) 54375						
	(B) 52375		x / 90°/	y 120°			
	(C) 54475						
	(D) 54365			z			





(A) essential

		EE-III Year	Sample Paper	IEO-2016		
15.	customer throws the politely and say, ""	ne money at the vend Thank you sir". The en he is so rude to you ing polite". onclusion?	lor. The vendor would jvendor's assistant asked	•		
16.	<ul> <li>In 1991, produce growers began using a new, inexpensive pesticide, provoking many objections that they would damage both the environment and the produce they were growing. However, the fears have proven unfounded as, though 1996, produce prices had dropped and no ill effects had been reported.</li> <li>Which of the following, if true, would be the strongest objection to the argument above?</li> <li>(A) Consumption of the produce declined from 1991 to 1993, but rose sharply from 1994 to 1996.</li> <li>(B) Several areas in which use of the pesticide was forbidden have also experienced a drop in produce prices.</li> <li>(C) The amount of produce grown in 1991 was larger than that of 1996.</li> <li>(D) The time since the beginning of the use of the pesticide has been too short to allow some of the predicted effects to occur.</li> </ul>					
17.	Choose the approp (A) Sojourn	riate antonym for the	bold word <b>Linger</b> (C) Condone	(D) Quilt		
18.	Find the proper meaning of the word given in bold letters  APP won the election <b>fair and square.</b> (A) Honestly (B) Falsely (C) Corruptedly (D) Unexpectedly					
19.	None but the rich can afford air travel. Some of those who travel by air become sick.  Some of those who become sick require treatment.  Choose the best conclusion:  (A) All the rich travel by air  (B) All the persons who travel by air become sick  (C) All sick persons travel by air  (D) Only rich can travel by air					
20.	•	slow's theory of nee	•	s the demand of the other demands are		

(B) basic


(C) final

(D) emotional



## **Section-II: Technical**

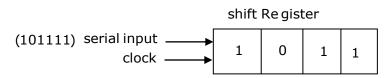
- 1. A bag contains 3 green and 2 red balls. A man draws 2 balls at random from the bag. If he is to receive 20paise for every green ball he draws and 10paise for every red one, what is his expectation (in paisa)?
  - (A) 32
- (B) 42
- (C) 52
- (D) 65
- 2. The contents of a four-bit register are initially 1011. The register is shifted six times to the right the serial input being 101111.



What are the contents of the register after six clock pulses?

- (A) 1110
- (B) 0111
- (C) 1111
- (D) 1011
- 3. Find out the maximum sine wave output voltage at 2MHz frequency, if the op-Amp slew rate is  $10~V/\mu s$  .
  - (A) 0.8V
- (B)  $\frac{2}{\pi}$  V
- (C)  $\frac{10}{2\pi}$  V
- (D) 0.4V

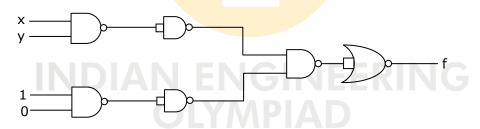4. In the following circuit, the output f is



- (A) xy
- (B) 0
- (C) 1
- (D) None of these


- 5. If  $f = x^n + y^n + z^n$ , then  $\nabla f \cdot r =$ 
  - (A) nf
- (B) f
- (C) n
- (D) 0
- The rotor resistance and standstill reactance of a 3-phase induction motor are respectively  $0.018\Omega$  and  $0.08\Omega$  per phase, normal slip at full load is 4%. Find the percentage reduction in stator voltage to develop full-load torque at half of full-load speed.
  - (A) 31.2%
- (B) 41.2%
- (C) 51.2%
- (D) 21.2%
- 7. If the above decoder is used only to display the numbers from 0 to 7(consider x, y, z as input variables) then what is the simplified Boolean expression (minimal sop) for the output line 'a'?
  - (A) y+xz+x'z'
- (B) y+x'z+xz'
- (C) x+vz+v'z'
- (D) x+y'z+yz'



- 8. A 4-pole series motor, when has its two field coils connected in parallel, runs at 1000 rpm. If the field coils are now connected in series keeping the supply voltage same and load torque same, the speed will
  - (A) remain same
- (B) halved
- (C) doubled
- (D)  $\frac{1}{\sqrt{2}}$  times
- 9. The slope in Ampere/Volt of the I<sub>D</sub>-V<sub>DS</sub> load-line for the circuit shown below is



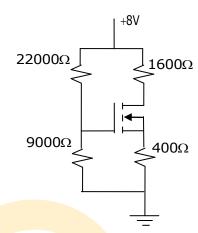- (B)  $\frac{-1}{1600}$
- (C)  $\frac{-1}{2000}$
- (D)  $\frac{-1}{31000}$



- 10. In CB's (circuit breakers), the peak value of restriking voltage is \_\_\_ and time taken to reach peak value is\_\_\_
- (A)  $V_{\rm m}, \frac{\pi}{2}\sqrt{\rm LC}$  (B)  $V_{\rm m}, \pi\sqrt{\rm LC}$ , (C)  $2V_{\rm m}, \frac{\pi}{2}\sqrt{\rm LC}$  (D)  $2V_{\rm m}, \pi\sqrt{\rm LC}$
- A generating station has got maximum demand of 40000 kW. What will be the cost per 11. kWh delivered, if the capital cost is Rs.  $95 \times 10^5$  annual cost of fuel & oil is Rs.  $9 \times 10^5$ and taxes, wages & salaries percentage Rs.  $6 \times 10^5$  and the rate of interest & depreciation is 10%. Annual load factor is 50%.
  - (A) 1.39 paise


(B) 13.9 paise

(C) 3.19 paise

(D) 0.139 paise

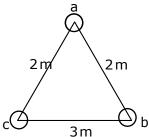12. 
$$Lt \left[ \frac{x^2 + 5x + 3}{x^2 + x + 2} \right]^x =$$


- $(A) e^4$
- (B)  $e^3$
- (D) e
- 13. The conductors of a three phase, 50Hz, 125 km long transmission line are as shown in figure. The diameter of each conductor is 0.6cm. What is the value of reactance per phase?



- (A)  $54.19\Omega$
- (B)  $64.19\Omega$
- (C)  $44.19\Omega$
- (D) 74.19Ω




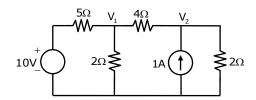14. Find the voltages  $V_1$  and  $V_2$  for the circuit shown below.




- (A) 0.6 V, 2.75 V
- (B) 2.7 V, 2.23 V
- (C) 5 V, 4 V
- (D) 0.2 V, 0.8 V
- 15. A synchronous machine is on infinite bus bar. When the prime mover is decoupled, how it will act as for excitation ON and OFF respectively?
  - (A) Alternator; Induction Generator
  - (B) Alternator; Induction Motor
  - (C) Synchronous Motor; Induction Generator
  - (D) Synchronous Motor; Induction Motor
- $\oint (xy + y^2)dx + x^2dy =$  where C is the closed curve of the region bounded by 16. y=x and  $y=x^2$ 
  - (A) 1/20
- (B) -1/20
- (C) 1/40
- (D) -1/40

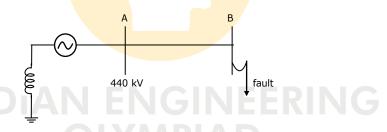17. Consider a P.S Network as shown in the figure



The P.U. equivalent of positive, negative, zero of the above Network is j0.2, j0.2, j0.34 and L-L-G fault occurred at bus 'B', the neutral voltage in kV in fault condition is \_\_\_\_\_, neutral reactance is j0.05.

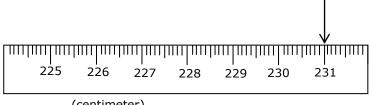- (A) 10 kV
- (B) 75 kV
- (C) 440 kV
- (D) 750 kV
- 18. Here as you can see the measured length ends before the mark of 231 cm. What can we say about the measured length with absolute confidence?



- (centimeter)
- (A)  $231cm \pm 0.1cm$

(B)  $230.9 \text{cm} \pm 0.1 \text{cm}$ 

(C)  $230 \text{cm} \pm 0.2 \text{cm}$ 

(D)  $231.1 \text{cm} \pm 0.1 \text{cm}$ 



- 19. Power in a  $1-\phi$  circuit is measured using an electrodynamometer wattmeter. resistance and inductance of wattmeter voltage circuit are  $2500\Omega$  and  $20\,\mathrm{mH}$ . At a frequency of 50 Hz and at a power factor of 0.3, the load voltage and load current are 120V and 10A respectively. The current coil has negligible inductance and a minimal resistance of  $0.2\Omega$ . What will be the % error in wattmeter reading when pressure coil is connected on the load side?
  - (A) 0.797%
- (B) 2.397%
- (C) 0.790%
- (D) 2.341%


- The solution for contour integral  $\oint_{|z|=1} e^{1/z} \sin \frac{1}{z} dz$  is 20.
  - (A) 2πi
- (B) πi
- (D) 5πi
- A Power Transformer (T/F) having 66/33 kV having Y /△ connection is protected by a 21. percentage differential protection. The CT ratio on L.V (Low voltage) side of the Transformer 400/1. What is the CT ratio on HV (High Voltage) side.
  - (A)  $\frac{200}{3}$

- (B)  $200\sqrt{3}$  (C)  $\frac{400}{3}$  (D)  $\frac{400}{\sqrt{3}}$
- An Ayrton shunt is designed to give the ammeter a current range of 1A,5A and 10A. If 22. the internal resistance of PMMC is  $50\Omega$  and full scale deflection current is 1mA. Find the values of the resistances in milli ohms?
  - (A) 5,5,39.9

(B) 6,6,49.9


(C) 9.5,8.5,50

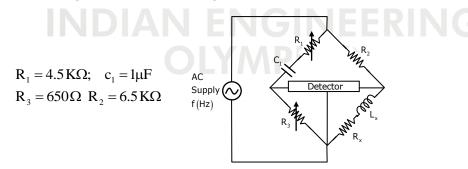- (D) 10.5,15,65.5
- 23. In the bridge shown here, the bridge elements are:



When the bridge is at balance condition for an supply angular frequency of 1000 rad/sec, The unknown resistance (in ohms) is

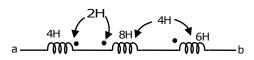
- (A) 894
- (B) 452
- (C) 529
- (D) 650
- Calculate the effective inductance of the following circuit. 24.



- (A) 24H
- (B) 22H
- (C) 18H
- (D) 10H



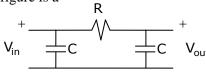- 25. The circuit shown in the following figure is a
  - (A) LPF
  - (B) HPF
  - (C) BPF
  - (D) APF




- A 2000/200 V,50 Hz, 1-phase transformer has an exciting current of 6A with core-loss of 250 W when LV side is excited with rated voltage. The no-load power factor and magnetizing component of current are
  - (A) 0.208, 5.87A

(B) 0.77, 6A

(C) 0.14, 4.28A

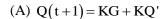
- (D) 0, 1.25A
- 27. A network diagram for a K G flip flop is shown below. The next state equation is



(B) 
$$Q(t+1) = KG + K'Q$$

(C) 
$$Q(t+1) = K'G + KQ'$$

(D) 
$$Q(t+1)=(G'+Q')k$$

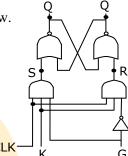


28. Two 6600/400V, 3-phase transformers X and Y having 250 KVA and 500 KVA respectively have the following particulars per phase when referred to the secondary side

$$X : R = 0.009 ; X=0.04 \Omega$$

Y: 
$$R = 0.004$$
;  $X=0.02 \Omega$ 

what will be the sharing of load of 600 KVA at 0.85 Pf lagging by x and y?

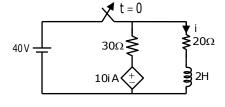- (A) X:199KVA, p.f=0.84(lag); Y:401KVA; p.f=0.845 (lag)
- (B) X:201KVA, p.f=0.81(lag); Y:399 KVA; p.f=0.84 (lag)
- (C) X:199KVA, p.f=0.85(lag); Y:401KVA; p.f=0.84 (lag)
- (D) X:201KVA, p.f=0.84(lag); Y:399 KVA; p.f=0.84 (lag)
- 29. In the circuit shown below, find the current i(t) for  $t \ge 0$  when the switch is opened at t = 0
  - (A)  $5e^{20t}A$
  - (B)  $2e^{-40t}A$
  - (C)  $5e^{-10t}A$
  - (D)  $2e^{-20t}A$



- 30. The circuit shown is based on ideal operational amplifier. It acts as a
  - (A) Substractor
  - (B) Adder
  - (C) Buffer
  - (D) Divider

