

PSG POLYTECHNIC COLLEGE, COIMBATORE - 641 004

**G12303 DIGITAL LOGIC DESIGN**

**Model Question Paper**

**Time: 3 Hours**

**Max.Marks: 100**

**Instructions:**

1. **Group A** and **Group B** questions should be answered in the Main Answer book.
2. Answer any **TEN** questions in **Group A**. Each question carries three marks.
3. Answer **ALL** questions either **(a)** subdivision or **(b)** subdivision in **Group B**. Each question carries 14 marks.

**Group – A**

**Marks: 10 x 3 = 30**

1. Write the advantages in operating as digital mode
2. Convert the following numbers into its decimal equivalent: (i)  $(314)_8$  (ii)  $(1011\ 1100)_2$
3. Perform the following division in binary;  $11011 / 101$
4. Construct the two basic gates using universal gates.
5. State and its prove deMorgan's theorem
6. Simplify the Boolean expressions to a minimum number of literals:  $xyz' + x'yz + x'yz'$ .
7. Draw the block diagram of 4X1 multiplexer and write its truth table.
8. Using k-map, find the simplified Boolean equation for the given values.  
 $F(a,b,c,d) = \Sigma(3,4,5,7,9,13,14,15)$
9. Design a half adder and simplify using K-map.
10. Define level triggering and edge triggering.
11. Show the characteristics equation for the complement output of JK flip flop is  
 $Q'(t+1) = J'Q' + KQ'$ .
12. Draw the logic diagram of 4 bit SIPO shift register
13. Give the number of bytes stored in the memories listed below: (i)  $8K \times 16$  (ii)  $2T \times 8$
14. Compare the EPROM & Flash Memory
15. Draw the internal organization diagram of a 64X4 RAM

**Group– B**

**Marks: 5 x 11 = 55**

16. a) (i) Convert the following binary numbers to hexadecimal & to binary (5)  
(1) 1.10010 (2) 110.010  
(ii) How many printing characters are there in ASCII? How many of them are special characters. (9)  
(OR)
- b) (i) Perform the subtraction on the given unsigned binary numbers using the 2's complement (5)  
(1) 10011-10001 (2) 100010-100011  
(ii) Represent the decimal number 5137 in (1) BCD (2) Gray code (3) ASCII (9)
17. a) (i) Express the Boolean function  $F = A + B'C$  as a sum of minterms. (5)

(ii) Find the complements of expression (1)  $(x'+y+z')(x+y')$  (9)

(OR)

b) With the circuit diagram, explain the principle of operation 2 input TTL NAND gate.

18. a) Construct a 16\*1 multiplexer with two 8\*1 and one 2\*1 multiplexers.

(OR)

b) Implement full adder with a decoder & NAND gates.

The adder inputs are A, B, C & D and the outputs are S & Co.

19. a) Construct a JK flip flop , using a D-Flip flop, a 2-1 line multiplexer, and an inverter.

(OR)

b) What is the difference between serial & parallel transfer? Which transfer method is the fastest one? Explain how to convert serial data to parallel.

20. a) Draw a PLA circuit to implement the following functions:

i)  $F1 = A'B + AC' + A'BC'$     ii)  $F2 = (AC + AB + BC)'$

(OR)

b) Explain in detail about the RAM.