



Name :
Roll No. :
Invigilator's Signature :

CS/B.TECH (BME)/SEP.SUPPLE/SEM-7/BME-703/2012

2012

POWER & CONTROL SYSTEM

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

i) The characteristics equation of a closed loop second order system is given as $s^2 + 4s + 16 = 0$ the resonant frequency in radian/sec of the system is

a) 2

b) $2\sqrt{3}$

c) 4

d) $2\sqrt{2}$.



ii) The unit step response of a network is $(1 - e^{-at})$ then the unit impulse response will be


- a) ae^{-at}
- b) $ae^{-\frac{t}{a}}$
- c) $\frac{1}{ae^{-at}}$
- d) $(1-a)ae^{-at}$.

iii) The Routh array of a characteristic equation is given below :

S^4	8
S^3	7
S^2	-3
S^1	2
S^0	1

The number of roots lying on the right hand side of s-plane is

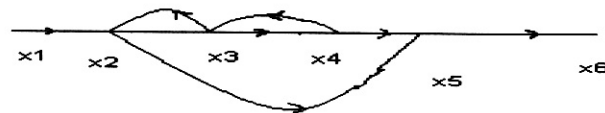- a) 1
 - b) 2
 - c) 3
 - d) 4.
- iv) The signal flow graph of a system is shown in the figure below. The number of forward path is



- a) 2
- b) 3
- c) 4
- d) 5.



v) For a unit step input, a system with forward path transfer function $G(s) = 20/s^2$ and feedback transfer function $H(s) = (s + 5)$ has a steady state output of

- a) 0
- b) 5
- c) 0.2
- d) 10.

vi) When the gain K of a system becomes zero, the roots of the loci

- a) move away from the poles
- b) move away from the zeros
- c) coincide with the poles
- d) coincide with the zeros.

vii) When cathode is more positive with respect to anode for a thyristor, the number of blocked PN junction is

- a) 1
- b) 2
- c) 3
- d) 4.

viii) A thyristor may be termed as

- a) DC switch
- b) AC switch
- c) either (a) or (b)
- d) square wave switch.

ix) $\frac{di}{dt}$ protection for an SCR is achieved by

- a) R in series with SCR
- b) L in series with SCR
- c) R across SCR
- d) L across SCR.



x) Most suitable solid state devices for audio, VHF/UHF and microwave amplifiers is

- a) IGBT
- b) S.I.T.
- c) MOSFET
- d) P.U.T.

xi) For a continuous conduction freewheeling diode conducts in a single semi converter for

- a) α
- b) $\beta - \Pi$
- c) $\alpha + \Pi$
- d) β .

xii) For a continuous conduction in a single phase semi converter each SCR conducts for

- a) α
- b) Π
- c) $\alpha + \Pi$
- d) $\alpha - \Pi$.

xiii) In a single phase full converter, if output voltage has peak and average value of 325V and 133V respectively, then the firing angle is

- a) 40°
- b) 140°
- c) 50°
- d) 130° .

xiv) Each diode of a 3-phase half wave diode rectifier conducts for

- a) 60°
- b) 120°
- c) 180°
- d) 90° .



xv) In a single phase full converter, the number of SCRs conducting during overlap is


- a) 1
- b) 2
- c) 3
- d) 4.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

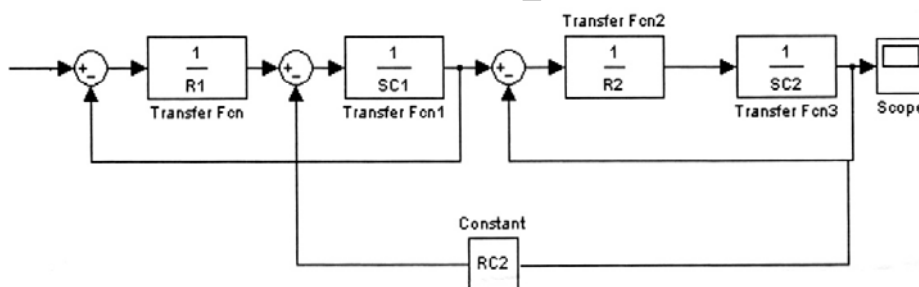- 2. Write short note on any *one* of the following :
 - i) Tachogenerator
 - ii) Error detector
 - iii) Synchro.
- 3. Find the overall transfer function of the system shown below :



Use block diagram reduction method.

- 4. State Nyquist stability criterion & define gain margin, phase margin from the nyquist plot.



5. Draw the Static characteristics of a SCR, along with proper labelling. Also explain the different operating regions.
6. What are the applications of rectifier ?
7. Explain the function of a step down chopper.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

8. A unity feedback control system has open loop transfer function $G(s) = \frac{k}{s(s+2)(s+5)}$. Sketch the root locus &

show

- a) Line for $\zeta = 0.5$ and value of k for this damping ratio.
- b) The frequency at which the root locus crosses the imaginary axis and the corresponding value of k .


$8 + 4 + 3$

9. a) Draw the unit step response of 2nd order underdamped system & define the following term :

Rise time, peak time, maximum peak overshoot, delay time, settling time.

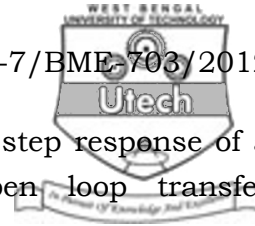- b) The open loop transfer function of a unity feedback system is $G(s) = \frac{k}{s(10+s)}$. Determine the gain of k so

that the system will have a damping ratio of 0.5. For this value of k determine settling time, peak time & peak overshoot.



c) Obtain the unit impulse response & step response of a unity feedback system whose open loop transfer function is $G(s) = \frac{(2s+1)}{s^2}$. 5 + 5 + 5

10. a) Define the term 'gain margin' & 'phase margin'.
 b) A unit feedback control system has open loop transfer function $G(s) = \frac{200(s+5)}{s(s+5)(s+20)}$. Sketch the bode plot & show the gain margin, phase margin, gain crossover frequency & phase cross over frequency. 4 + 7 + 4

11. a) Explain the two transistor analogy of a thyristor and derive an expression for the anode current using this analogy.
 b) Explain briefly different communication process of SCR.
 c) What is G.T.O. ?
 d) Define holding and latching current of SCR. 7 + 5 + 1 + 2

12. Explain the principle of Chopper operation. Discuss the control strategies of chopper. What are the applications of chopper ? Classify choppers. 5 + 5 + 5

13. What is inverter ? What is a rectifier ? Explain the function of a single phase half controlled rectifier using inductive load. What do you mean by free-wheeling diode ? What happens if a free-wheeling diode is connected to the circuit of single phase half controlled rectifier having inductive load ? 1 + 1 + 1 + 5 + 1 + 6

=====