



INDIAN ENGINEERING
OLYMPIAD (IEO)


Indian Engineering Olympiad

Sample Questions for Round 1 (IEO - 2019)

IEO Round 1 test will be an 30 mins online tests where students can attempt the test from their laptop, Tab, Mobile etc. Student can take the online Test from their Home or any nearby cyber cafe.

Electrical / Electronics / Instrumentation Engineering

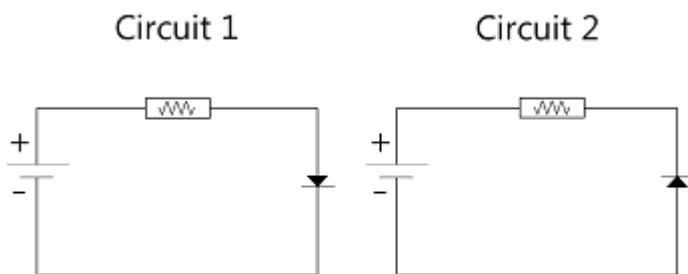Q1) In which of the circuits will electrical current flow?



- A) Circuit 1
- B) Circuit 2
- C) Both Circuits
- D) None

Q2) The difference in electric potential between two points is called:

- A) Electricity
- B) Volt
- C) Voltage
- D) Electric Power

Content Partner McGraw Hill Education.

IEO-2019
Partners & Sponsors:



School of
Engineering





INDIAN ENGINEERING
OLYMPIAD (IEO)

Indian Engineering Olympiad

Sample Questions for Round 1 (IEO - 2019)

IEO Round 1 test will be an 30 mins online tests where students can attempt the test from their laptop, Tab, Mobile etc. Student can take the online Test from their Home or any nearby cyber cafe.

General Aptitude

1. When 0.26 is written in the simplest fractional form, the sum of the numerator and the denominator is:
(A) 73 (B) 43 (C) 63 (D) None of these
2. Two alarm clocks ring their alarms at regular intervals of 40 seconds and 44 seconds respectively. If they first beep together at 1 PM, at what time will they beep again together?
(A) 3 minutes 20 seconds past 1
(B) 12 minutes 44 seconds past 1
(C) 1:07 p.m.
(D) 7 minutes 20 seconds past 1

Content Partner McGraw Hill Education.

IEO-2019
Partners & Sponsors:

